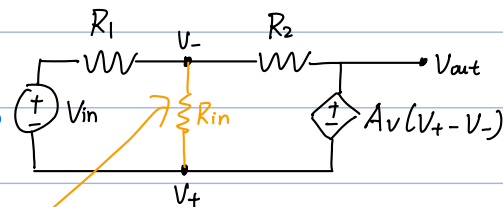



Opamp

1. A_v $V_{out} = A_v (V_+ - V_-)$

E. in. amp. $V_{out} = -A_v V_- \stackrel{\dots}{=} \frac{-R_2/R_1}{1 + \frac{1+R_2/R_1}{A_v}} V_{in}$
 n.in. amp. $\stackrel{\dots}{=} \frac{1 + R_2/R_1}{1 + \frac{1+R_2/R_1}{A_v}} V_{in}$



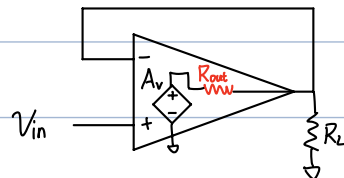2. Output R E. opamp buffer $V_{out} \stackrel{\dots}{=} \frac{A_v}{(1+A_v) + \frac{R_o}{R_L}} V_{in}$



3. Input R $V_- \xrightarrow{R_{in}} V_+$

E. ia. $V_{out} = -A_v V_- \stackrel{\dots}{=} -A_v V_{in} \frac{R_2/R_1}{1 + A_v + \frac{R_2/R_1}{R_{in} + R_1}}$



R_{in} no effect (feedback ^{Miller} amplifies it by A_v)

General A_v $R_{in} = \frac{V_{TEST}}{I_{TEST}}$, same for R_{out}

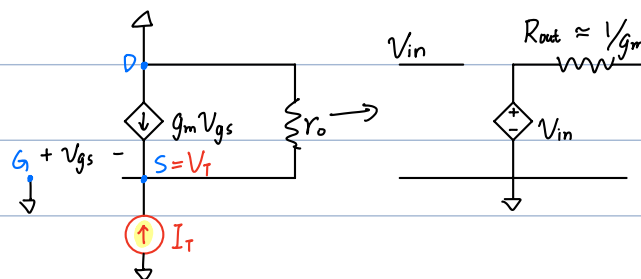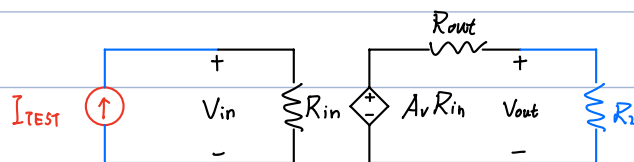E. ss R_{out} of follower

$$I_T + g_m V_{gs} + \frac{V_{gs}}{r_o}, \quad V_T = -V_{gs}$$

$$R_{out} \stackrel{\dots}{=} \frac{1}{g_m + 1/r_o} \approx \frac{1}{g_m}$$



4. I_{bias} (for BJT base, tiny for MOS)

$$\stackrel{\sim 500n}{I_B} = \frac{I_{B1} + I_{B2}}{2}$$

$$\stackrel{\sim 50n}{I_{os}} = |I_{B1} - I_{B2}|$$


E. nia. I_{B2} harmless, but $V_{out} \stackrel{\text{superpos}}{=} V_{in} (1 + \frac{R_2}{R_1}) + I_{B1} R_2$

sln. add R_3 to V_+

When $V_{in} = 0 \xrightarrow{\text{want}} -I_{B2} R_3 (1 + \frac{R_2}{R_1}) + I_{B1} R_2 = 0$

if $I_{B1} = I_{B2}$, $R_3 \stackrel{\dots}{=} R_1 \parallel R_2$

(DC R_{eq} seen at V_-)

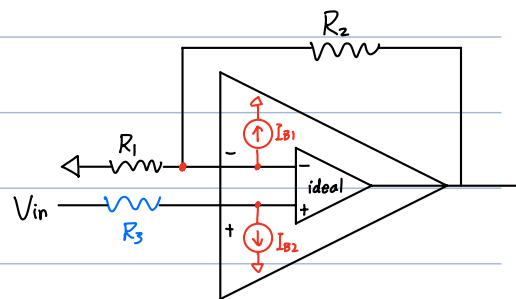


Always have input -DC gnd path for I_B to flow

5. V_{os} (any terminal) null offset

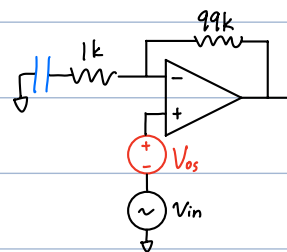E. nia $V_{out} = 100 (V_{in} + V_{os})$

sln. kill DC gain w/ cap $\frac{1}{2\pi(1k)C} \ll f$

PC: unity gain, AC: normal $\rightarrow V_{out} = 1 V_{os} + 100 V_{in}$



6. I_{out} clipping, indep. of V_{in} , V_{SS} (feedback R included)


if L_{arge} : RC problem, noise $1k \sim 100k$

7. BW $2p/z$ C_{in} doesn't matter (V_{in} ideal)

$A_{v1,2}$ in form $g_m R_{out}$

if phase shift = 180° when gain $\geq 1 \rightarrow$ oscillate und
unity neg. feedback (neg + $180^\circ \rightarrow$ pos)


Sim. compensate to shift ω_{p2} , ω_z

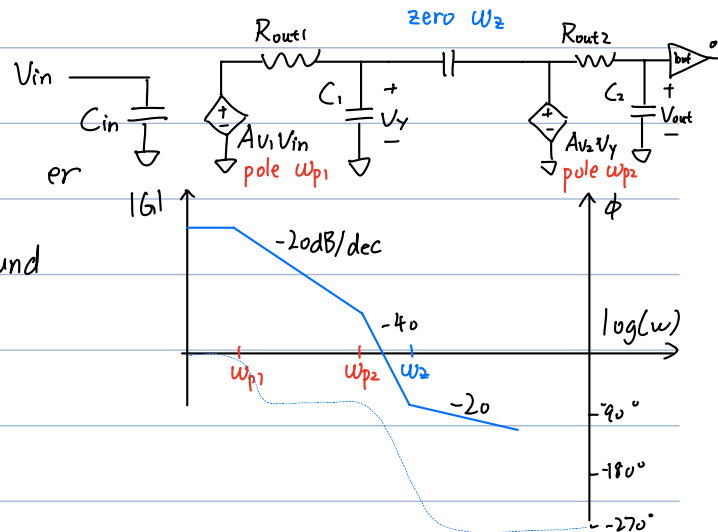

Single-pole (RC) $A_v = \frac{A_o}{1 + j\omega/\omega_o}$, $\omega_o = \frac{1}{RC}$

unity gain freq $\omega_t = \omega_o A_o \approx \omega A(j\omega)$ (if $\omega \gg \omega_o$)

gain-BW product: $\omega_o A_o$

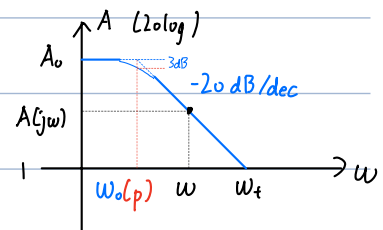


E. nia w/ $A_v(j\omega)$ limit

$$G_v(j\omega) = \frac{1 + R_2/R_1}{1 + \frac{1 + R_2/R_1}{A_v(j\omega)}} = \frac{1 + R_2/R_1}{1 + \frac{j\omega(1 + R_2/R_1)}{A_o \omega_o}} = \frac{1 + R_2/R_1}{1 + j\omega/\omega_{pole}}$$

$$A_v(j\omega) = \frac{A_o}{1 + j\omega/\omega_o}$$

$$\omega_{pole} = \omega_{3dB} = \frac{A_o \omega_o}{1 + R_2/R_1} = \frac{\omega_t}{1 + R_2/R_1}$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

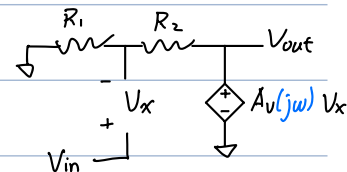

clsd. loop curve bounded by open-loop gain, turning at ω_{3dB} (vs ω_o at open)

$$GBW > G_v \cdot \omega_{max}$$


E. ia: gain = $-\frac{R_2}{R_1}$, but BW (ω_{3dB}) same: $\frac{\omega_t}{1 + R_2/R_1}$

8. slew rate (non linear) limits $\frac{dV_{out}}{dt}$ (BW)

A_1 can't steer fast enough $\rightarrow i$ held on one side

if ΔV large, first stage outputs i_{max} (bias mirror)
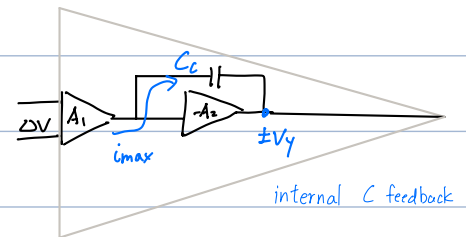
$$\text{slew rate} \equiv \frac{dV}{dt} = \frac{i_{max}}{C_c}$$



E. nia w/ step input $V_o u(t) \rightarrow$


$$v_o(t) = V_o \left(1 + \frac{R_2}{R_1}\right) \left(1 - e^{-t/\tau}\right)$$

$$\tau = \frac{1}{\omega_{3dB}} = \frac{1 + R_2/R_1}{\omega_t}$$

$$\dot{v}(t) = \frac{V_o (1 + R_2/R_1)}{\tau}$$

if $<$ slew rate \rightarrow linear

if $>$ \rightarrow slew (straight line)

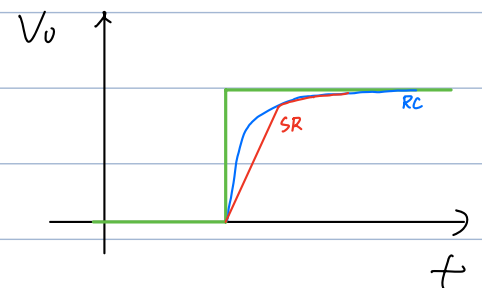


9. CM

$$V_{cm} = \frac{1}{2}(V_A + V_B) \quad V_{id} = V_A - V_B$$

$$V_{out} = A_{dm} V_{id} + A_{cm} V_{cm}$$

$$CMRR \equiv \frac{A_{dm}}{A_{cm}} \left\{ \begin{array}{l} \text{open-loop} \\ \text{once } A_{dm} \text{ closed, } A_{cm} \downarrow \end{array} \right.$$

E. nia

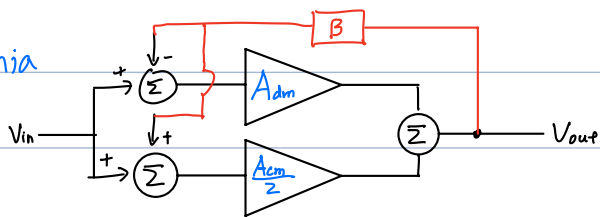

$$\begin{aligned} V_{out} &= A_{dm} (V_{in} - \beta V_{out}) + \frac{A_{cm}}{2} (V_{in} + \beta V_{out}) \\ &= V_{in} \frac{A_{dm} + \beta A_{cm}/2}{1 + \beta(A_{dm} - A_{cm}/2)} \\ &\approx V_{in} \left(\frac{1}{\beta} + \frac{1}{2\beta CMRR} \right) \quad \left(\beta = \frac{1}{G_v} \right) \end{aligned}$$

w/ opamp A_{cm}


E. diff. amp.

$R_1 = R_2 = R_3 = R_4$, opamp w/ nonideal CMRR, let inputs have V_{cm} , $V_{id} = 0$

$$V_{out} = A_{dm} (V_+ - V_-) + \frac{A_{cm}}{2} (V_+ + V_-)$$

$$= A_{dm} \left(\frac{V_{cm}}{2} - \left(\frac{V_{cm}}{2} + \frac{V_{out}}{2} \right) \right) + \frac{A_{cm}}{2} \left(\frac{V_{cm}}{2} + \left(\frac{V_{cm}}{2} + \frac{V_{out}}{2} \right) \right)$$
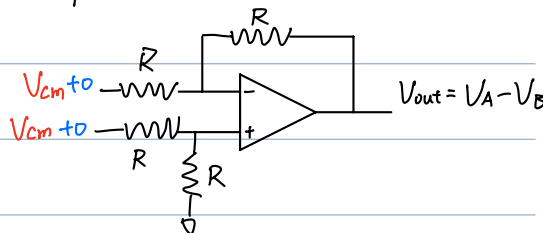
$$\Rightarrow \frac{\frac{1}{2} A_{cm} V_{cm}}{1 + \frac{A_{dm} - A_{cm}}{2}} \approx \frac{V_{cm}}{CMRR}$$




ideal opamp

E. R variation \rightarrow diff amp amplifies V_{cm} !

E. Accelerometer


3 parallel plates

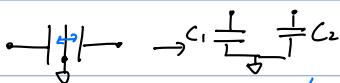

1. middle plate can move under acceleration $\rightarrow C_1 \neq C_2$

2. Drive w/ $V_1 = V_2 = V_{ref}$. Then shut V_{ref} and hold it

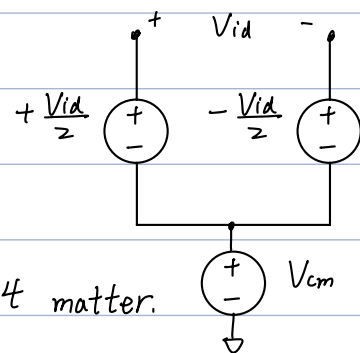3. If plate moves further $\rightarrow C_1 \downarrow, V_1 \uparrow, V_2 \downarrow \rightarrow$ gets Δ , init doesn't matter.



Single supply

Can +/- all input voltages, decouple I/O

want $V_{in} = 4.5V$ (divided), no DC I

C_2 kills DC gain ($=1$), AC gain = 100

C_{big} filter AC noise from source

DC unity gain w/ $V_{out} = V_{in} = 4.5V$, $V_{LOAD} = 0$

AC $V_+ = V_{in} \frac{R_s}{R_s + R_{big}}$, $V_{out} = 100 V_{in} = V_{load}$

