

Analysis

P/M! +/- feedback!

Design DOF \gg # constraints

E. $\frac{V_o}{V_i} = -\frac{R_2}{R_1} \frac{1}{1+sC_L R_2}$




$f_{LP} = \frac{1}{2\pi R_2 C_L}$ R need \downarrow

Noise (*) R generate thermal noise $\overline{V_n^2} = 4kTR\Delta f$ \rightarrow bw

Q: thermal $\rightarrow \overline{V_{n_{eq}}^2} \sim \Delta f$ + flicker $\sim \frac{1}{f}$

$\overline{V_{out}^2} = \overline{V_{n_1}^2} \left(\frac{R_2}{R_1}\right)^2 + \overline{V_{n_2}^2} + \overline{V_{n_{eq}}^2} \left(1 + \frac{R_2}{R_1}\right)^2$

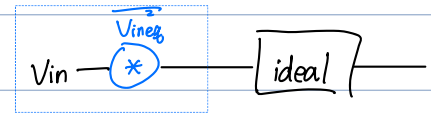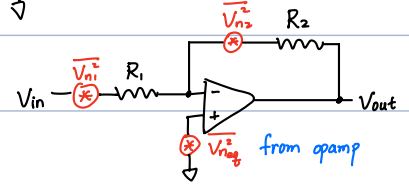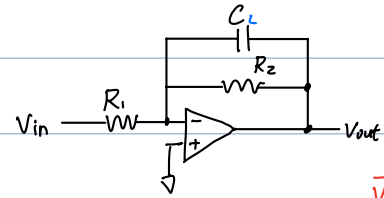$\overline{V_{out}^2} = 4kT\Delta f (R_1 G^2 + R_2) + \overline{V_{n_{eq}}^2} (1+G)^2$
 $\overline{V_{n_{eq}}^2} = \frac{\overline{V_{out}^2}}{G^2} = 4kT R_1 \Delta f \left(1 + \frac{1}{G}\right) + \overline{V_{n_{eq}}^2} \left(1 + \frac{1}{G}\right)^2$



\therefore need $V_{in} > \overline{V_{n_{eq}}^2}$; $R \downarrow$, $\Delta f \downarrow$

$\Delta f \downarrow \rightarrow$ want perfectly enclose signal when filtering $\rightarrow C_2 \uparrow$

$\therefore \downarrow, C \uparrow \rightarrow \overline{V_{out}^2} \downarrow \rightarrow$ power \uparrow

if need $G \uparrow$, $R_2 \uparrow$, $C \downarrow$, $\overline{V_{out}^2} \uparrow$, $SNR = \frac{(G V_{in})^2}{\overline{V_{out}^2}} = \text{same}$ (if $G \gg 1$)

single-ended .vs. differential ($V_d(t) = V_1(t) - V_2(t)$)

Opamp C amplifier

volt $A_v = A_{oc} \left(\frac{R_i}{R_i + R_s}\right) \left(\frac{R_2}{R_L + R_o}\right)$




Assume unilateral: $i \rightarrow 0$; but actually bilateral \rightarrow 2-port model

ni find intersection of load line (V_{out} vs $V_p - V_N$)

positive feedback \rightarrow Schmitt trigger

$V_p - V_N = \frac{R_1}{R_2 + R_1} V_{out} - V_{in}$


$\equiv +\beta V_{out} - V_{in}$

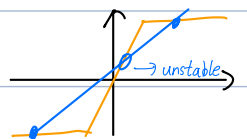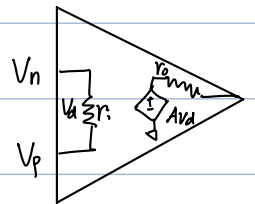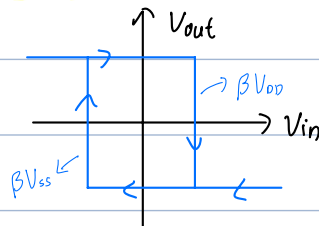

when $V_{in} > 0$, but $V_+ > V_{in} > 0$

need $V_{in} > V_+ = \beta V_{out}$ to switch

Feedback

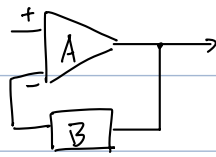

$$G = \frac{V_o}{V_i} = \frac{A}{1+A\beta}$$

$\xrightarrow{\text{error factor}}$

$$= \frac{1}{\beta} \frac{T}{1+T}$$

$T \equiv A\beta$ (loop gain)

$$\approx \frac{1}{\beta} \quad \text{if } T \gg 1$$

gain \rightarrow control

CR easier to control than opamp A)


Desensitivity

$$\frac{\Delta G}{G} = \frac{1}{1+T} \frac{\Delta A}{A} \approx \frac{\Delta \beta}{\beta}$$

$$E. S_{out} = \frac{A}{1+\beta A} (S_{in} + S_{d1} + \frac{S_{d2}}{A_1} + \frac{S_{d3}}{A_1 A_2})$$

\rightarrow better bw

\rightarrow attenuated by preceding gains

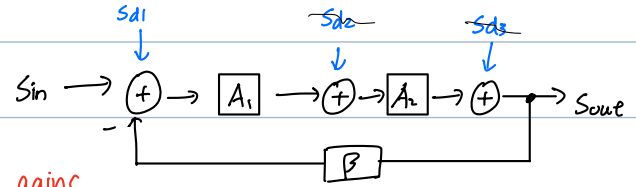

Analysis 1. find if feedback

a. find feedback type (V/I?)

b. + / - feedback?

c. find fwd path & back network

d. find the right two-port eq. for the network


type:	i/o	v	i
		(aka II)	
	v	series-shunt	sr-sr
	i	sh-sh	sh-sr

E. ni $S_{in} = V_{in} \rightarrow$ series measure

$S_{out} = V_{out} \rightarrow$ shunt measure



$$S_{fb} = V_- = \frac{R_1}{R_1 + R_2} V_{out}$$

$$S_E = S_{in} - S_{fb} = V_+ - V_-$$

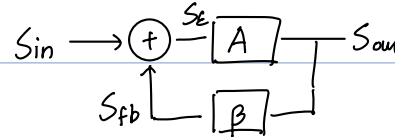

$$\frac{S_{out}}{S_{in}} = \frac{A}{1+\beta A}$$

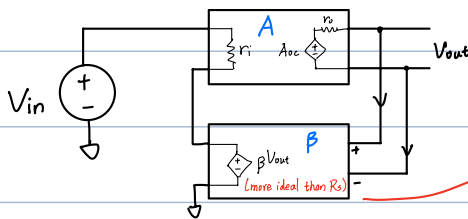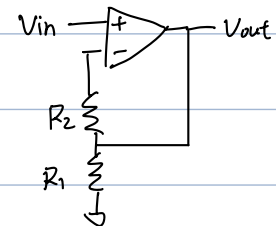
$$\frac{S_E}{S_{in}} = \frac{1}{1+\beta A}$$



Need Th eq. circuit w/ a VCVS

indep. VC \rightarrow CS in ; dep. VS \rightarrow VS out

Two-port Test w/ other indep. src.

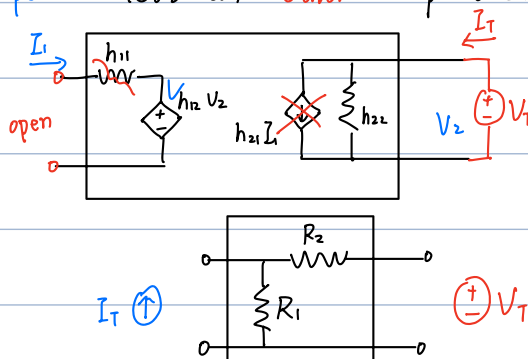


$$R_T = \frac{V_1}{I_1} = h_{22} = R_1 + R_2 = h_{22}$$

$$V_1 = V_T \frac{R_1}{R_1 + R_2} = h_{12} V_T$$


$$h_{12} = \frac{R_1}{R_1 + R_2}$$
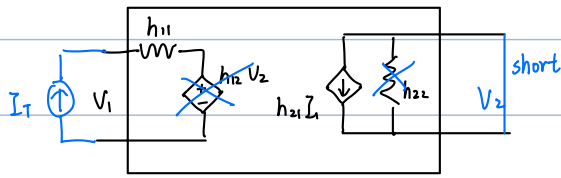
$$\begin{cases} V_1 \equiv h_{11} I_1 + h_{12} V_2 \\ I_2 \equiv h_{21} I_1 + h_{22} V_2 = \frac{V_{out}}{R_1 + R_2} \end{cases}$$




$$V_1 = I_{\text{test}} h_{11} = I_{\text{test}} (R_1 \parallel R_2) \rightarrow h_{11} = \frac{R_1 R_2}{R_1 + R_2}$$
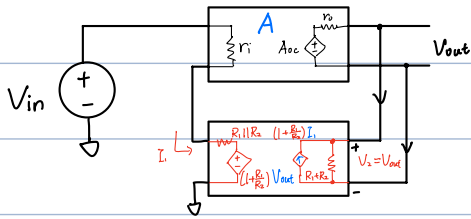
$$I_2 = h_{21} I_T = -\frac{R_1}{R_1 + R_2} I_T \rightarrow h_{21} = -\frac{R_1}{R_1 + R_2}$$




V_{fb} is only \diamond output!

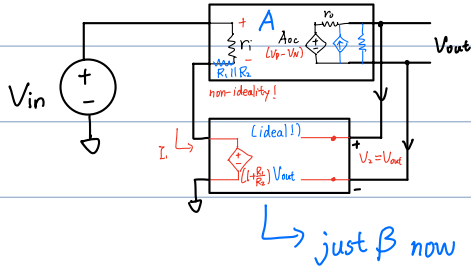

if $r_i \gg (R_1 \parallel R_2)$, input loaded

The $(1 + \frac{R_1}{R_2}) I_1$ \diamond suggest **feedforward**

\hookrightarrow just β now

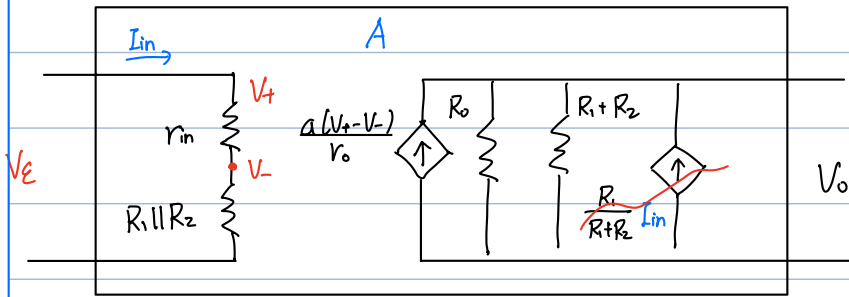


$$I_{in} = \frac{V_E}{r_{in} + R_1 \parallel R_2} \quad V_p - V_n = \frac{r_{in}}{r_{in} + R_1 \parallel R_2} V_E$$

$$A_{eg} = \frac{V_o}{V_E} = \frac{1}{V_E} \left(\frac{a(V_p - V_n)}{r_o} + \frac{R_1}{R_1 + R_2} I_{in} \right) (R_o \parallel (R_1 + R_2))$$


$$= \left[\frac{a r_{in} / r_o}{r_{in} + R_1 \parallel R_2} + \frac{R_1}{R_1 + R_2} \cdot \frac{1}{r_{in} + R_1 \parallel R_2} \right] (r_o \parallel (R_1 + R_2))$$

since $a \frac{r_{in}}{r_o}$ large!
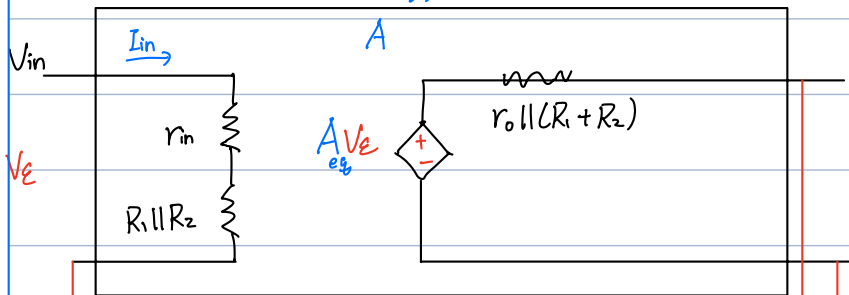
$$A_{eg} \approx a \text{ if } r_{in} \rightarrow \infty, r_o \rightarrow 0.$$


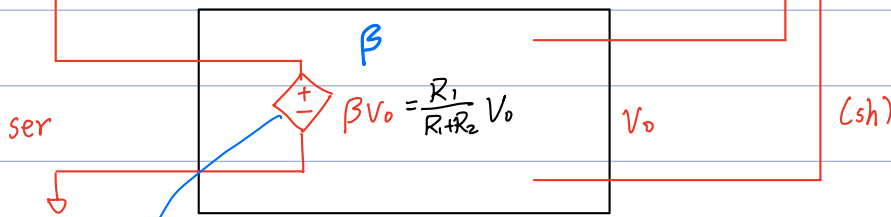
$$V_o = A_{eg} V_E, \text{ hiding } (V_p - V_n)$$




$$\beta = \frac{V_{fb}}{V_o} = \frac{R_1}{R_1 + R_2}$$

$$\text{Open loop gain} = \frac{V_o}{V_{in}} \Big|_{V_{fb}=0} = A_{eg} \approx a \frac{r_{in}}{r_{in} + (R_1 \parallel R_2)} \frac{R_1 + R_2}{r_o + R_1 + R_2}$$

$$\text{Loop gain} = A_{eg} \beta$$

$$\text{Closed loop gain} = \frac{V_o}{V_{in}} = \frac{A_{eg}}{1 + A_{eg} \beta} \rightarrow \frac{1}{\beta}$$

Imp

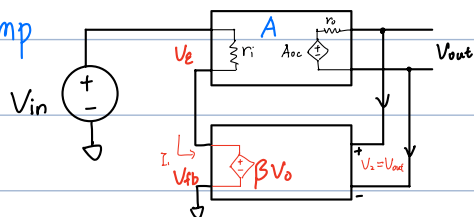

$$G = \frac{V_{out}}{V_{in}} : \text{closed loop gain}$$

assume small g_{12} (unilateral)

shunt (V out measure)


1. V_T (open out) $V_E = \frac{V_o}{A_{oc}} = \frac{V_T}{1 + \beta A_{oc}}$

$$i_T = \frac{1}{r_{in}} \frac{V_T}{1 + \beta A_{oc}} \rightarrow R_{in} = r_{in} (1 + \beta A_{oc}) \rightarrow \text{feedback strengthens } R_{in} :)$$

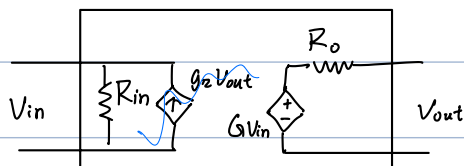2. V_T (gnd in) $V_E = -\beta V_T$

$$i_T = \frac{V_T - A_{oc} V_E}{r_o}$$

$$= \frac{V_T}{r_o} (1 + \beta A_{oc}) \rightarrow R_{out} = \frac{r_{out}}{1 + \beta A_{oc}}$$




For any feedback network w/ A (r_i, r_o) and β

$$G = \frac{A_{oc}}{1 + \beta A_{oc}}$$

$$R_{in} = R_{in} (1 + \beta A_{oc}) \quad \left. \vphantom{R_{in}} \right\} \text{for ser-sh}$$

$$R_{out} = R_{out} (1 + \beta A_{oc})^{-1} \quad \left. \vphantom{R_{out}} \right\}$$

Sh-sh

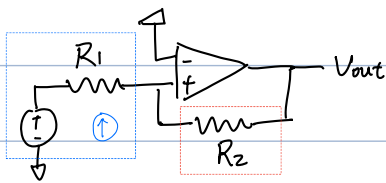


$$S_{out} = V_{out}$$

(shunt)

$$S_{in} = I_{in}$$

(shunt addition of V_{in} and V_{fb})




sh-sh

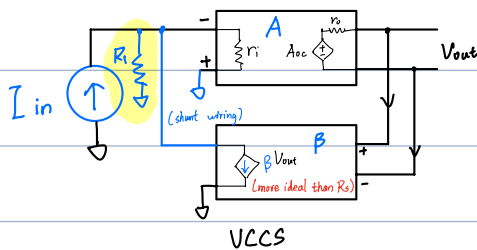


symmetry \rightarrow

$$y_{12} = -\frac{1}{R_2} = y_{21}$$

$$y_{22} = R_2 = y_{11}$$

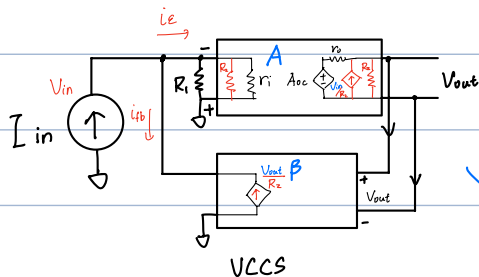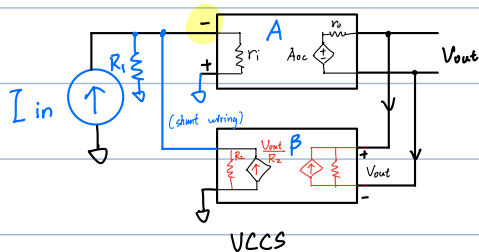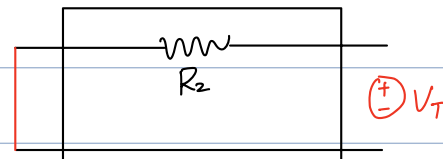
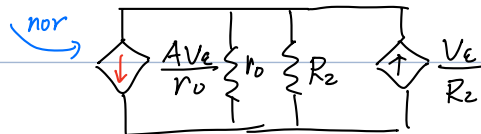
$$V_E = (R_1 \parallel R_2 \parallel R_{in}) i_E$$




$$\rightarrow R_{eq} = r_o \parallel R_2$$

$$I_{eq} = V_E \left(\frac{1}{R_2} - \frac{a}{r_o} \right)$$

$$V_o = V_E \left(\frac{1}{R_2} - \frac{a}{r_o} \right) (r_o \parallel R_2)$$


$$V_{in} = -V_E$$

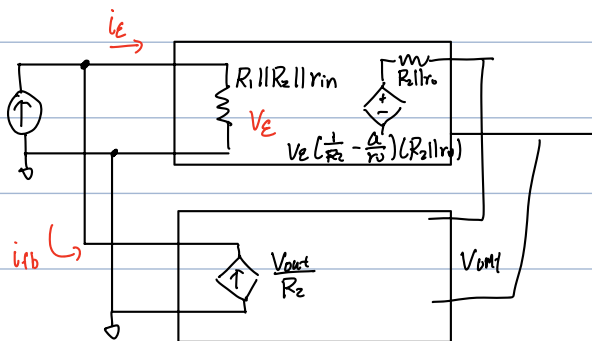


$$A_{eq} = \left(\frac{1}{R_2} - \frac{a}{r_o} \right) (R_2 \parallel r_o) (R_1 \parallel R_2 \parallel R_{in})$$

$$\beta = \frac{1}{R_2}$$

$$G = \frac{A_{eq}}{1 + \beta A_{eq}}$$

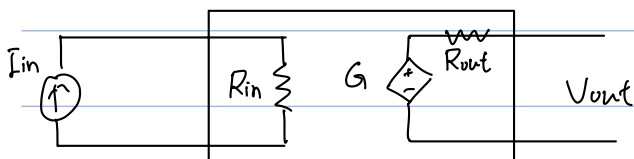

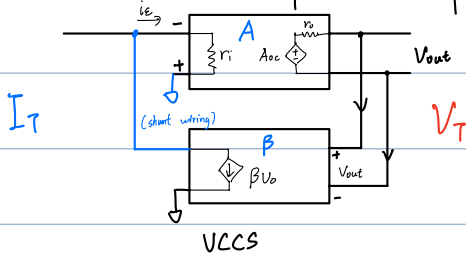$i \rightarrow v$ (sh-sh) (transimpedance amp)




$$R_{in} \equiv \frac{r_{in}}{1 + \beta A_{oc}}$$

$$R_{out} \equiv \frac{r_{out}}{1 + \beta A_{oc}}$$



- Summary
1. identify I/O \rightarrow ser/sh
 2. draw ideal feedback config.

E3. VCCS


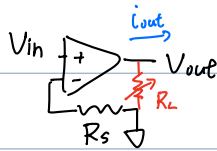


ser-ser

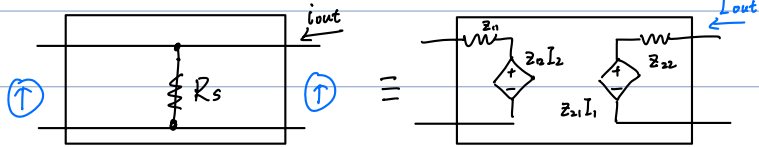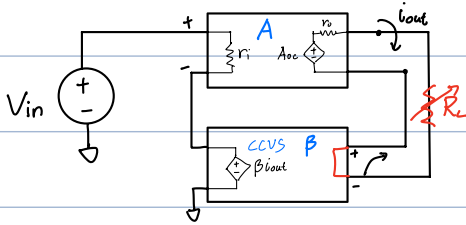assume $V_p = V_n$: $i_{out} = \frac{V_{in}}{R_s}$ indep. of load R_L (can be E. a diode)



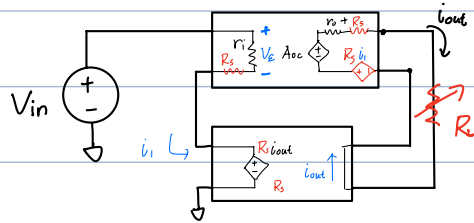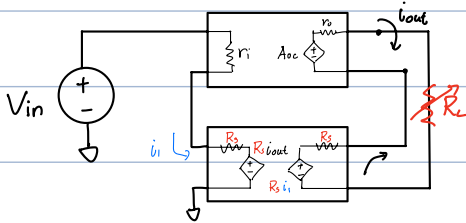Apply symmetrical $I_T \rightarrow z_{22} = R_s = z_{11}$
 $z_{12} = R_s = z_{21}$



$$i_1 = \frac{V_p - V_n}{r_{in}}$$

